

1. ✓ What is transformer?

⇒ Transformer is a static device that transforms electric power from one circuit to another without change of frequency. There is no rotating part in a transformer. So it is a static device. Transformer operates on ac supply. In transformer operation two electrical circuits are not connected to each other. They are interlinked by common magnetic circuit.

2. Define an ideal transformer.

⇒ An ideal transformer is an imaginary transformer, which has

- i) no copper losses (no winding resistance)
- ii) no iron loss in core
- iii) no leakage flux.

An ideal transformer gives output power exactly equal to the input power. The efficiency of an ideal transformer is 100%. Actually it is impossible to have such a transformer in practice. but ideal transformer makes problems easier.

Zero winding resistance:- It is assumed that resistance of primary as well as secondary winding of an ideal transformer is zero. Both the coils are purely inductive in nature.


No leakage flux:- Leakage flux is a part of magnetic flux which does not get linked with secondary winding. In ideal transformer it is assumed that entire amount of flux get linked with secondary winding.

100% efficiency:- An ideal transformer does not have any losses like hysteresis loss, eddy current loss etc.

3. Write a short note on Auto Transformer.

⇒ ~~An auto-winding~~ auto transformer is a single winding transformer in which a part of the winding

is common high voltage to low voltage.

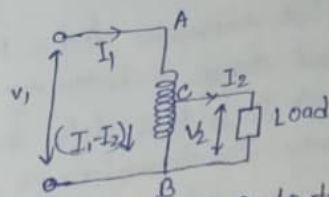

step down auto transformer

The primary winding AB has  $N_1$  number of turns and the secondary winding BC has  $N_2$  number of turns. BC is common to primary and secondary winding.

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = K \quad [K \text{ is the turns ratio}]$$

The input current is  $I_1$  and  $I_2$  load current is  $I_2$ . Then  $I_1 N_1 = I_2 N_2$ . The output voltage  $V_2$  can be varied.

4. Explain the operating principle of Transformer.

⇒ Transformer works on principle of inductance between two or more inductively coupled coils.

Here one of the winding is called primary, which is energized by an alternating voltage source and secondary winding is connected to the load. If ac voltage is supplied to primary winding coil and produce alternating current, alternating magnetic flux in the core of the transformer. Alternating magnetic flux links with primary and secondary coil turns and induces an emf by self induction and mutual induction respectively.

5. & 6 & 7. Derive expressions for the emf induced in the transformer windings?



From Faraday's law

$$E_1 = -N_1 \frac{d\phi}{dt}$$

$$= -N_1 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= -N_1 \omega \phi_m \cos \omega t$$

$$= N_1 \omega \phi_m \sin(\omega t - \pi/2)$$

The induced emf lags flux by  $\pi/2$ .  $\omega \rightarrow$  Question-7

$$E_{1 \text{ max}} = N_1 \omega \phi_m$$

$$= N_1 2\pi f \phi_m [W = 2\pi f]$$

$$E_{1 \text{ max}} = \frac{N_1 \omega \phi_m}{\sqrt{2}} = \frac{N_1 2\pi f \phi_m}{\sqrt{2}}$$

$$= \sqrt{2} \pi f N_1 \phi_m$$

$$E_1 = 4.44 f N_1 \phi_m \quad \omega \rightarrow \text{Question-6}$$

$$E_2 = 4.44 f N_2 \phi_m$$

Similarly

$$\frac{E_2}{E_1} = \frac{4.44 f N_2 \phi_m}{4.44 f N_1 \phi_m}$$

$$\Rightarrow \frac{E_2}{E_1} = \frac{N_2}{N_1} = K \quad \omega \rightarrow \text{Question-5}$$

8. Why is a transformer rated in KVA?

$\Rightarrow$  The rated capacity of a transformer is expressed in KVA. Generally the rating of a transformer is determined by its temperature. The temperature is caused by the losses in the machine. Copper loss depends on the value of the load current and iron loss on voltage. Total loss of a transformer depends on volt-ampere. It is independent of load power factor. A certain amount of current will produce at any value of power factor. The output in kilowatts is proportional to the power factor. The load current increases proportionally to losses and temperature.

9) What will happen if a transformer is operated in DC?  
⇒ Transformers work on Faraday's law of Electro magnetic Induction which current in coil must change. If DC is applied current will not change and transformer will not work.

Winding resistance is very small. For DC, inductive reactance is zero and frequency is zero. Therefore, impedance is low. Winding ~~name~~ draws more current which may damage the winding.

10) Why will a transformer not operate under DC supply?

⇒ We know that transformer operation principle is based on Faraday's law of Electro magnetic Induction.

We state that whenever there is a change of flux linkage in coil and EMF is induced in the coil. When DC is applied in the primary coil of transformer there will be no change of flux in the coil. So no EMF will be induced in the primary coil there.

11) Why is the core of a transformer laminated? Transformer core is made up of which material?

⇒ The core is not designed to have any currents flow through it. However, a conducting loop that experience a changing magnetic field. It is small current induced in it. These called eddy current.

The core is laminated to reduce these currents to a minimum interfere with the efficient transfer of energy from the primary coil to secondary coil.

Transformer core is made up

Soft iron.


12) Explain with reasons as to why transformer core is made up of Silicon steel lamination

⇒ A transformer core is made up of Silicon steel lamination because

1. It helps to reduce energy losses through eddy currents
2. The laminations stack together to form an efficient magnetic circuit, reducing the core size and weight.
3. Silicon steel is a good electrical conductor and has a high magnetic permeability, which helps to increase the transformer's efficiency.

4. The laminations also act as insulation between the turns of the transformer's winding.

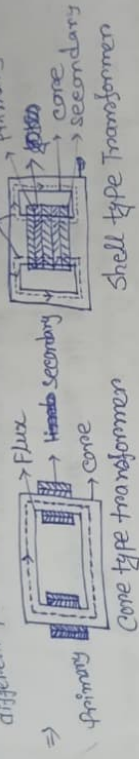13. Draw a core type and shell type transformer, mention their different parts and make a comparison the two types of transformers



Core type	Shell type
i) two limbs and two joints	i) three limbs and two joints
ii) single magnetic circuit	ii) Two magnetic circuits
iii) more copper loss	iii) Less copper loss
iv) percentage impedance Lower	iv) percentage impedance higher

14) Distinguish between core type and shell type transformer?

Core type

Shell type

- |   |  |
|---|--|
| i) Easy in design and construction.                         | i) comparatively complex.                              |
| ii) Reduction of leakage reactance is not easily possible.  | ii) Reduction of leakage reactance is highly possible. |
| iii) The assembly can be easily dismantled for repair work. | iii) Cannot be easily dismantled for repair work.      |




15) Why is the low voltage winding placed near the core?  
 → The winding and core are both made of metals so the winding has to be placed in between them. The thickness of insulation depends on the voltage rating.

An insulation of winding is placed near to the transformer core of the winding. If HV winding is required to insulate them, the result more insulation is required material and also size increase in the cost of insulation. Reduce the cost of insulation of transformer increases. the low voltage winding placed near the core.

16) What are the ideal conditions of a transformer operation?

- ⇒
- i) The two windings of this transformer have no resistance.
  - ii) There are, no losses, to the resistance, eddy current and hysteresis.
  - iii) The efficiency of the transformer is 100%.
  - iv) The total flux generated in the transformer is confined to the core and leakage flux is zero.

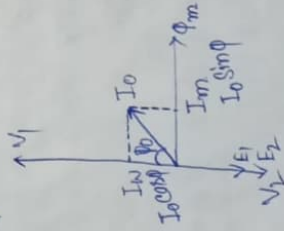17) Draw and explain the no load phasor diagram of an ideal single-phase transformer.



NO load primary current  $I_0$  is called the exciting current of the transformer.

1. one in phase with  $V_1$  known as iron loss component  $I_w$  because it supplies the iron loss.

$$I_w = I_0 \cos \phi_0$$

2. The other component is in quadrature  $V_1$  and is known as magnetizing component  $I_m$ .

$$I_m = I_0 \sin \phi_0$$


When the transformer is no load, current lags  $V_1$  and an angle  $\phi_0$

$$V_0 = V_1 I_0 \cos \phi_0$$

It is principle the core loss which is responsible for the shift in current vector from  $90^\circ$  position, angle  $\phi_0$  is known as hysteresis angle.

$$I_0 = \sqrt{I_w^2 + I_m^2}$$

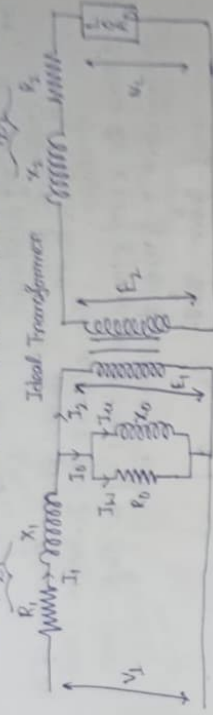18) Draw the exact equivalent circuit of a transformer and describe briefly the various parameters involved in it.




- leakage flux is present at primary and secondary sides.
- The leakage reactance are denoted  $X_1$  and  $X_2$  respectively
- The primary and secondary winding resistance denoted as  $R_1$  and  $R_2$  respectively. These resistances cause voltage drop as  $I_1 R_1$  and  $I_2 R_2$  and also copper losses  $I_1^2 R_1$  and  $I_2^2 R_2$
- Permeability of the core cannot be infinite. magnetizing current is needed. Mutual flux also causes core loss in iron parts of the transformer.
- The no load current  $I_0$  is divided pure inductance  $X_0$  and non inductive resistance  $R_0$  which are connected into parallel across the primary.

The voltage transformation ratio,

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = K$$

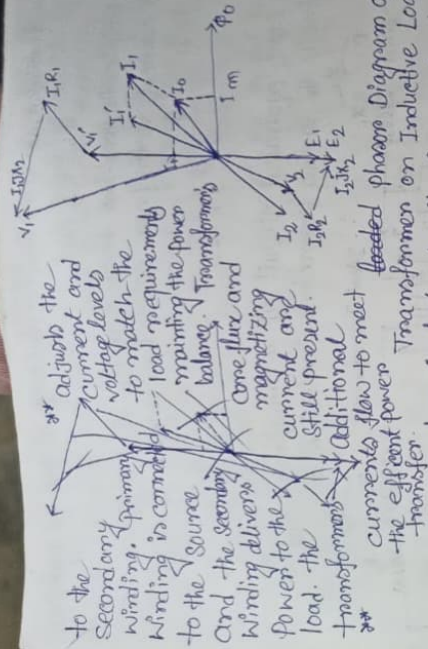19. Explain the principle of operation of a transformer under loaded condition.
- ⇒ Under loaded conditions, a transformer operates by transferring electrical energy from the primary winding



20) Draw the exact equivalent circuit of a single-phase transformer referred to primary side.

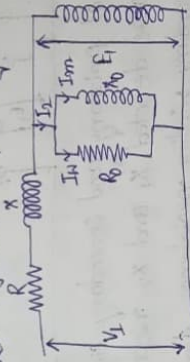


Fig:- Primary side equivalent side

21) Draw the exact equivalent circuit of a single-phase transformer under lagging P.f load and describe briefly the various parameters involved in it.

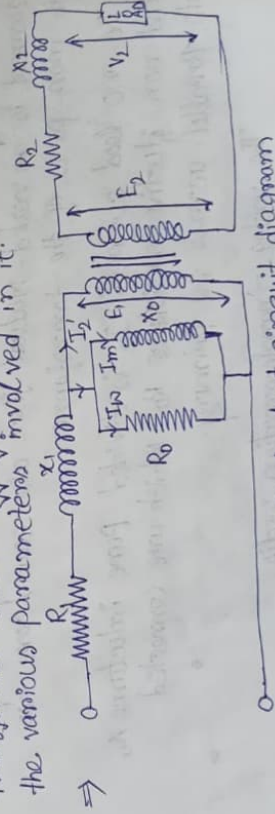


Fig:- Equivalent circuit diagram

Where

$R_1$  = primary winding resistance

$R_2$  = secondary winding resistance

$I_0$  = No-load current


$I_m$  = magnetizing component




This  $I_w$  and  $I_0$  are connected in parallel across the primary circuit. The value of  $E_1$  (Primary e.m.f) is obtained by subtracting vectorially  $I_1 Z_1$  from  $V_1$ . The value of  $X_0 = E_1/I_0$  and  $R_0 = \frac{E_1}{I_w}$ , we know that

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = K$$

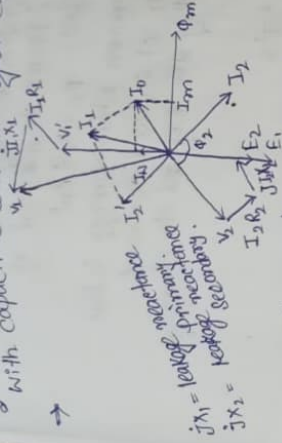23) Draw the phasor diagram of a Transformer of a Transformer with capacitive load and again explain.



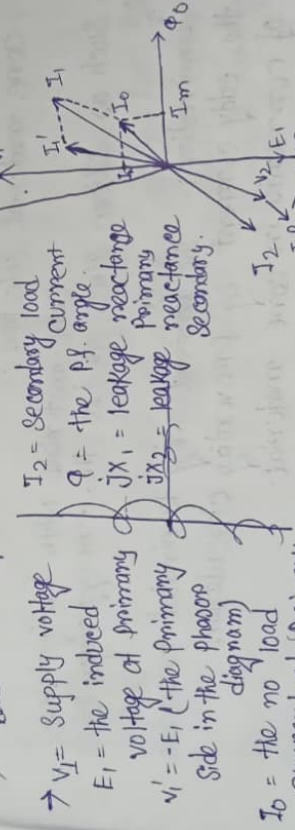22) & 24) Draw the phasor diagram of a Transformer with inductive load and explain?



25) Explain the energy losses in a transformer.

26) Copper Losses (ohmic Losses):

These losses occur due to the ohmic resistance of the transformer windings and dissipated a heat if  $I_1$  and  $I_2$  is primary and secondary resistance. Then the copper losses will be  $I_1^2 R_1$  and  $I_2^2 R_2$





For get max efficiency

$$\begin{aligned} & \frac{d}{dI_2} (V_2 I_2 \cos \phi_2 + \omega i + I_2^2 R_e) - V_2 \cos \phi_2 - V_2 I_2 \cos \phi_2 (V_2 \cos \phi_2 + 2 I_2 R_e) = 0 \\ & \Rightarrow \frac{d}{dI_2} (V_2 I_2 \cos \phi_2 + \omega i + I_2^2 R_e) - V_2 \cos \phi_2 - V_2 I_2 \cos \phi_2 (V_2 \cos \phi_2 + 2 I_2 R_e) = 0 \\ & \Rightarrow \frac{d}{dI_2} (I_2 R_e + \frac{P_i}{I_2}) = 0 \\ & \Rightarrow R_e - \frac{P_i}{I_2^2} = 0 \\ & P_i = I_2^2 R_e \end{aligned}$$

Iron loss = copper loss

This is the condition for max efficiency.

Define voltage regulation of a transformer.


$$\left[ \frac{\text{Secondary no voltage} - \text{Secondary full load voltage}}{\text{Secondary no load voltage}} \right] \times 100\%$$

$E_2$  = the secondary no load voltage.  
 $V_2$  = the terminal voltage at secondary.

$$\frac{E_2 - V_2}{E_2} \times 100$$

single-phase transformer

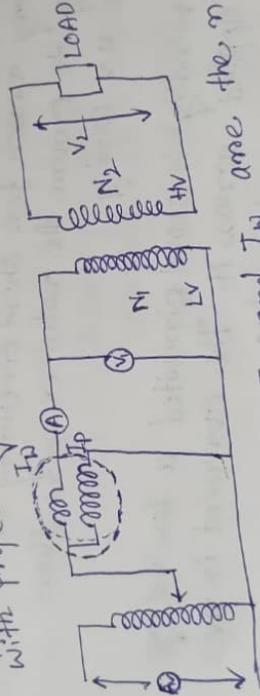33) Explain the open circuit test of transformer with proper diagram.



$I_m$  and  $I_w$  are the no load components.

$V_1$  = primary voltage  
 $V_2$  = secondary voltage

$R_0$  = core loss resistance

$X_0$  = magnetizing reactance

$I_w = N_1$  = primary winding

$N_2$  = secondary winding

$$P_i = W_0 - \frac{V_1^2}{R_0} - I_0^2 R_0$$

$\frac{V_1^2}{R_0}$  and  $I_0^2 R_0$  are very small, so.

$$P_i = W$$

$$\therefore W = V_1 I_0 \cos \theta$$

$$\cos \theta = \frac{W}{V_1 I_0}$$

34) Explain why the open test gives core loss and short circuit test gives copper loss.

→ The open circuit is conducted to the <sup>core</sup> loss in a transformer. When the secondary winding is kept open, the primary winding is connected to the rated voltage. In this condition the core loss includes hysteresis and eddy current losses in the transformer.

The short circuit test is performed to determine the copper losses in a transformer. When the secondary winding is short-circuited, and the rated voltage is applied to the primary winding. Secondary winding represents the total current to magnetize the core and the current flowing through the copper winding, by subtracting you can obtain the copper loss.

Explain why L.V. winding is short circuited and H.V. winding is excited for the short circuit test of single phase transformer.

35) L.V. winding short-circuited  
The primary reason for short circuiting the L.V. winding to ensure the rated current flows through the H.V. winding.

The L.V. winding is short circuited a low voltage eght is applied across it. The current in the H.V. winding to its rated value.

H.V. winding short circuited

A rated voltage apply the H.V. winding to helps the determining the copper losses in the transformer.

The short-circuited L.V. winding allows for a practical and safe measurement of the current.



- 38) A single-phase transformer with a 2 kVA rating has a 480 V primary and a 120 V secondary. Determine, to primary and secondary full-load currents of the transformer.

→ Single phase transformer VA rating = 2 kVA

$$= 2 \times 1000$$

$$\text{Primary voltage } (V_1) = 480 \text{ V}$$

$$\text{Primary load currents} = \frac{2000}{480}$$

$$= 4.16 \text{ A}$$

$$\text{Secondary voltage } (V_2) = 120 \text{ V}$$

$$\text{Secondary load currents} = \frac{2000}{120}$$

$$= 16.66 \text{ A}$$

- 39) A single phase transformer with a 2 kVA rating has 30 primary turns and 350 secondary turns. The net cross-sectional area of the core is  $250 \text{ cm}^2$ . The primary winding is connected to the 230 V, 50 Hz supply. Calculate a) the peak value of flux density in the core b) the primary current when the secondary current is 100 A.

⇒

Single phase transformer,

$$\text{Primary turns } (N_1) = 30$$

$$\text{Secondary } (N_2) = 350$$

$$\text{Cross sectional area } (A) = 250 \text{ cm}^2$$

$$= 250 \times 10^{-2} \text{ m}^2$$

$$\text{Voltage } (E) = 230 \text{ V}$$

$$\text{Frequency } (f) = 50 \text{ Hz}$$

We know,

$$\Phi_m = B_m \times A$$

$$= B_m \times 250 \times 10^{-2} \text{ Wb/m}^2$$

∴ Again,

$$E = 4.44 \Phi_m f N_1$$

$$\frac{230}{4.44} = \frac{E}{4.44 \Phi_m f N_1}$$

$$1.38 \times 10^{-6}$$

$$\Rightarrow 230 = 4.44 \times B_m \times 250 \times 10^{-2} \times 50 \times 30$$

$$\Rightarrow B_m = \frac{230}{4.44 \times 250 \times 10^{-2} \times 1500}$$

$$= \frac{1.38 \times 10^{-6} \text{ Wb/m}^2}{1.38 \times 10^{-6}}$$

ii) we know,

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{I_1}{100} = \frac{350}{20}$$

$$\Rightarrow I_1 = \frac{3500}{20}$$

$$= 175 \text{ A}$$

The primary current is 175 A.

4) The primary of a 50 Hz, step down transformer has 480 turns and is fed from 6400V supply. Find a) the peak value of the flux produced in the core, b) the voltage across the secondary winding if it has 20 turns.

a)  $f = 50 \text{ Hz}$

$N_1 = 480$

$E_1 = 6400 \text{ V}$

$E_1 = 4.44 \phi f N_1$

$\Rightarrow 6400 = 4.44 \times \phi \times 50 \times 480$

$\Rightarrow \phi = \frac{6400}{4.44 \times 50 \times 480}$

$= 0.06 \text{ Wb}$

b)  $\frac{E_1}{E_2} = \frac{N_1}{N_2}$

$\Rightarrow \frac{6400}{E_2} = \frac{480}{20}$

$= 24$

$\Rightarrow E_2 = \frac{6400}{24}$

$= 266.6 \text{ V}$

41) A 5KVA, 440/220 V single phase transformer has a primary and secondary winding resistances are 2 ohms and 0.8 ohms respectively and the corresponding leakage reactances are 10 ohms and 15 ohms respectively. Find the secondary terminal



voltage at full load, 0.8 power factor lagging

$$\begin{aligned} \text{voltage rating} &= 5 \text{ kVA} \\ &= 5 \times 10^3 \text{ VA} \\ \text{voltage (V)} &= \frac{5000}{\sqrt{3}} = 2886.75 \text{ V} \\ \text{resistance (R)} &= \frac{220}{440} = 0.5 \Omega \end{aligned}$$

$$\begin{aligned} 1.5 \times 10^3 \text{ VA} \\ 440 \text{ V} \\ 1.5 \times 10^3 \text{ VA} \\ 440 \text{ V} \\ 1.5 \times 10^3 \text{ VA} \\ 440 \text{ V} \end{aligned}$$

$$\text{voltage rating} = 5 \text{ kVA} = 5 \times 10^3 \text{ VA}$$

$$\text{current (I)} = \frac{5000}{440} = 11.36 \text{ A}$$

$$\text{primary resistance (R}_1\text{)} = 2 \Omega$$

$$\text{secondary resistance (R}_2\text{)} = 0.8 \Omega$$

leakage reactance,

$$\text{primary reactance (X}_1\text{)} = 10 \Omega$$

$$\text{secondary reactance (X}_2\text{)} = 1.5 \Omega$$

$$R_{00} = 2 \times \left( \frac{220}{440} \right)^2 + 0.8 = 10 \times \left( \frac{220}{440} \right)^2 + 1.5$$

$$= 0.5 + 0.8$$

$$= 1.3 \Omega$$

$$I_2 = \frac{5 \times 10^3}{220}$$

$$= 22.73 \text{ A}$$

WE KNOW,

$$E_2 = V_2 + I_2 R_{02} \cos \phi_2 + I_2 X_{02} \sin \phi_2$$

$$V_2 = 220 - I_2 R_{02} \cos \phi_2 + I_2 X_{02} \sin \phi_2$$

$$= 220 - 22.73 \times 1.3 \times 0.8 + 22.73 \times 1.5 \times 0.6$$

$$= 220 - 22.73 \times (1.04 + 2.4)$$

$$= 220 - 78.19$$

$$= 141.81 \text{ V}$$

4) A 200 kVA single phase transformer has 1000 turns in the primary and secondary winding resistances are 2 ohms and 0.8 ohms respectively and the corresponding leakage resistances are 10 ohm and 1.5 Ohms respectively.

Find the secondary terminal voltage at full load.  
0.8 power factor lagging.

$$\Rightarrow \frac{kVA}{N_p f} = \frac{200}{1000}$$

42) A 200 KVA single phase transformer has 1000 turns in the primary and 600 turns on the secondary. The primary winding is supplied from a 440 V, 50 Hz source. Find the secondary voltage at no load.

$\therefore$  primary and secondary currents at the full load.

$\Rightarrow$  Single phase transformer.

$$\text{Voltage rating} = 200 \text{ KVA} \\ = 200 \times 10^3 \text{ VA}$$

$$\text{Primary winding } (N_p) = 1000$$

$$\text{Secondary } (N_s) = 600$$

$$\text{Voltage } (E) = 440 \text{ V}$$

$$\text{Frequency } (f) = 50 \text{ Hz}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{400}{E_2} = \frac{1000}{600}$$

$$\Rightarrow 10 E_2 = 2400$$

$$\Rightarrow E_2 = 240$$

$\therefore$  Primary current

$$V_1 I_1 f = VA$$

$$\Rightarrow 440 \times I_1 \times 50 = 200 \times 10^3$$

$$\Rightarrow I_1 = \frac{200 \times 10^3}{440 \times 50}$$

$$\frac{20000}{12.8}$$

$$= 9.09 \text{ A}$$

Secondary current.


$$V_2 I_2 f = VA$$

$$\Rightarrow 240 \times I_2 \times 50 = 200 \times 10^3$$

$$\Rightarrow I_2 = \frac{200 \times 10^3}{240 \times 50} = 166.6 \text{ A}$$

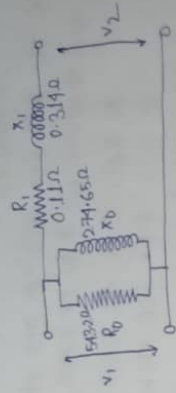43) Obtain the equivalent circuit parameters of a 8 kVA, 220/440V, 50 Hz single phase transformer having following test results are

O.C. test : Primary voltage 220V  $I = 0.9A$   $W = 90W$   
 S.C. :  $x = 20$   $I = 15A$   $W = 100W$



1st case for O.C. test :-

$$V = 220V$$

$$I = 0.9A$$

$$P = 90W$$

We know,  $P = VI \cos \theta$

$$\Rightarrow \cos \theta = \frac{P}{VI} = \frac{90}{220 \times 0.9} = 0.45$$

$$\sin \theta = \sqrt{1 - \cos^2 \theta} = \sqrt{1 - (0.45)^2} = \sqrt{1 - 0.2025} = 0.89$$

$$R_0 = \frac{V_1}{I_0 \cos \theta_0} = \frac{220}{0.9 \times 0.45} = 543.2 \Omega$$

$$X_0 = \frac{V_1}{I_0 \sin \theta_0} = \frac{220}{0.9 \times 0.89} = 274.65 \Omega$$

2nd case for S.C. test

$$V = 20V$$

$$I = 15A$$

$$P = 100W$$

$$R_{0H} = \frac{P}{I^2} = \frac{100}{(15)^2} = 0.44 \Omega$$

$$Z_{0H} = \frac{20}{15} = 1.33 \Omega$$

$$X_{0H} = \sqrt{(1.33)^2 - (0.44)^2} = \sqrt{1.25} \Omega$$



$$R_1 = 0.44 \times \left( \frac{220}{440} \right)^2$$

$$= 0.11 \Omega$$

$$X_1 = 1.25 \times \left( \frac{220}{440} \right)^2$$

$$= 0.314 \Omega$$

4) The following readings are obtained for open circuit and short circuit tests on 8 kVA, 400/120 V, 50 Hz Transformer

OC Test: 120 V, 4 A, 75 W

SC Test: 9.5 V, 20 A, 110 W

Calculate equivalent circuit parameters referred to high voltage side.

OC test:  $V = 120 \text{ V}$

$$I = 4 \text{ A}$$

$$P = 75 \text{ W}$$

We know,  $P = VI \cos \theta$

$$\therefore \cos \theta = \frac{P}{VI}$$

$$= \frac{75}{120 \times 4}$$

$$= 0.156$$

$$\sin \theta = \sqrt{1 - (0.156)^2}$$

$$= \sqrt{1 - 0.0225}$$

$$= \sqrt{0.9775}$$

$$= 0.988$$

$$R_0 = \frac{V}{I_0 \cos \theta} = \frac{120}{4 \times 0.156} = \frac{120}{0.624} = 192.30 \Omega$$

$$X_0 = \frac{V}{I_0 \sin \theta} = \frac{120}{4 \times 0.988} = \frac{120}{3.952} = 30.36 \Omega$$

SC test:


$$V = 9.5 \text{ V}$$

$$I = 20 \text{ A}$$

$$P = 110 \text{ W}$$

$$R_{\text{eff}} = \frac{P}{I^2} = \frac{110}{20^2} = \frac{110}{400} = 0.275$$
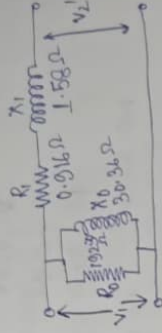
$$Z_{0H} = \frac{V}{I} = \frac{9.5}{20} = 0.475$$



$$R_1 = 0.275 \times \frac{400}{120}$$

$$= 0.916 \Omega$$

$$X_1 = 0.475 \times \frac{400}{120}$$

$$= 1.58 \Omega$$

45. The following readings are obtained for open circuit and short circuit tests on 20 kVA, 2000/200 V, 50 Hz single phase transformer.

OC Test :- 200 V, 1 A, 120 W

SC Test :- 60 V, 10 A, 300 W

1) Find efficiency at half load and 0.8 power factor lagging

⇒ For short circuit test,

$$Z_{01} = \frac{60}{10} = 6 \Omega$$

$$R_{01} = \frac{300}{(10)^2} = 3 \Omega$$

$$X_{01} = \sqrt{(6)^2 - (3)^2}$$

$$= \sqrt{36 - 9}$$

$$= \sqrt{27}$$

$$= 5.19$$

$$\frac{20 \times 10^3}{200} = \frac{20 \times 1000}{200}$$

$$= 100 \text{ A}$$

2) Rated current on the h.v. side =  $300 \times \left(\frac{100}{10}\right)^2$

$$= 300 \times 100$$

$$= 30000 \text{ W}$$

Iron loss = 120 W

Efficiency at half load and 0.8 power factor lagging is

$$= \frac{20 \times 10^3 \times 0.8 \times \frac{1}{2}}{20 \times 10^3 \times 0.8 \times \frac{1}{2} + \left(\frac{1}{2}\right)^2 \times 30000 + 120}$$

$$= \frac{8000}{8000 + 120 + 75} = 0.9762$$

$$= 97.62\%$$

$$= \frac{1}{1.7620} = 0.000131$$

$$= 0.0131\%$$

$$P_i = x^2 P_{Cu}$$

$$\Rightarrow 120 = x^2 \times 300$$

$$\Rightarrow x^2 = \frac{120}{300}$$

$$x = \sqrt{\frac{120}{300}} = 0.632$$

$$\eta_{\max} = \frac{0.632 \times 20 \times 10^3 \times 0.8}{0.632 \times 20 \times 10^3 \times 0.8 + 120 + 120 (0.632)^2 \times 300}$$

$$= \frac{10112}{10112 + 120 + 115.82}$$

$$= 0.9768$$

$\eta_{\max} = 97.68\%$  test data of a 50 kVA, 2400/120

4) The open circuit phase transformer are  
50 Hz single phase voltage 120 V,  $I = 9.65$  A.  
W = 396 W  
O.C. test :- primary voltage

Find equivalent circuit parameters.

$$\Rightarrow \cos \phi = \frac{P_o}{V_p I_c} = \frac{396}{9.65 \times 120} = 0.341$$

$$\therefore \theta = 70$$

$$\sin \phi = 0.93$$

$$\text{magnetizing current } (I_m) = I_m \sin \phi$$

$$= 9.65 \times 0.93$$

$$= 9.06 \text{ A}$$

$$\text{core loss } (I_c) = I_c \cos \phi$$

$$= 9.65 \times 0.341$$

$$= 3.29 \text{ A}$$

$$R_{eq} = \frac{V_p}{I_c} = \frac{120}{3.29} = 36.46 \Omega$$

$$X_{ml} = \frac{V_p}{I_m} = \frac{120}{9.06} = 13.24 \Omega$$